

6th Semester Diploma Engineering Examination, 2019

Full Marks : 100

Subject : Power Electronics and Drives

Subject Code : PED-12232

Time : 3 Hours

Pass Marks : 40

Answer in your own words.

Answer five questions in which Question No. 1 is compulsory and answer any four from rest questions.

All questions carry equal marks.

1. Fill in the blanks:

(a) A thyristor possesses _____ $p-n$ junction.

(b) The latching current is _____ than the holding current

(c) I.G.B.T. stands for _____.

(d) The output obtained from a rectifier is _____ in nature

(e) Choppers are used in _____.

(f) The process of turning of a conducting thyristor is called _____.

(g) The ripple frequency of the output wave form is _____ times the supply frequency in the case of three phase full converter.

(h) A motor in which rotor runs in discrete movement called _____.

(i) An inverter is a _____ converter.

(j) A converter can be used as a _____.

2. Explain the construction and working of a SCR. Also draw its $V-i$ characteristics and label the important points.

3. (a) Discuss classifications of Inverters.

(b) What is a D.C. servomotor? Explain. φ

4. (a) What are the methods of output voltage control of a $1-\phi$ inverter? \checkmark

(b) Compare $3-\phi$ and $1-\phi$ converters.

5. Explain single phase fully controlled bridge converter with $R-L$ load. Also draw the wave form.
6. (a) What are the different methods of turning on the SCR? Explain.
(b) Explain working principle of chopper.
7. Explain, how the speed of a DC series motor can be controlled using thyristor? How can this control circuit be modified for reversing the direction of rotation of motor?
8. Write short notes on any two of the following:
- (a) AC servomotor
 - (b) Cyclo converters
 - (c) Pulse width modulation
 - (d) Step up chopper